

date: 2025-01-23

# TFE4188 - Introduction to Lecture 2

## ICs and ESD

# Goal

Understand the **real-world** constraints on our IC

Understand why you must **always handle ESD** on an IC

# The real world constrains our IC

# What blocks must our IC include?

A BJT-based CMOS Temperature Sensor with Duty-cycle-modulated Output and  $\pm 0.54\text{ }^{\circ}\text{C}$  (3-sigma) Inaccuracy from  $-40\text{ }^{\circ}\text{C}$  to  $125\text{ }^{\circ}\text{C}$ .

Pin	Function	in/out	Value	Unit
VDD_3V3	analog supply	in	3.0	V
VDD_1V2	digital supply	in	1.2	V
VSS	ground	in	0	V
CLK_1V2	clock	in	20	MHz
RST_1V2	digital	out	0 or 1.2	V
I_C	bias	in	?	uA?
PHI1_1V2	digital	out	0 or 1.2	V
PHI2_1V2	digital	out	0 or 1.2	V
DCM_1V2	digital	out	0 or 1.2	V

[course plan](#)

# One more thing

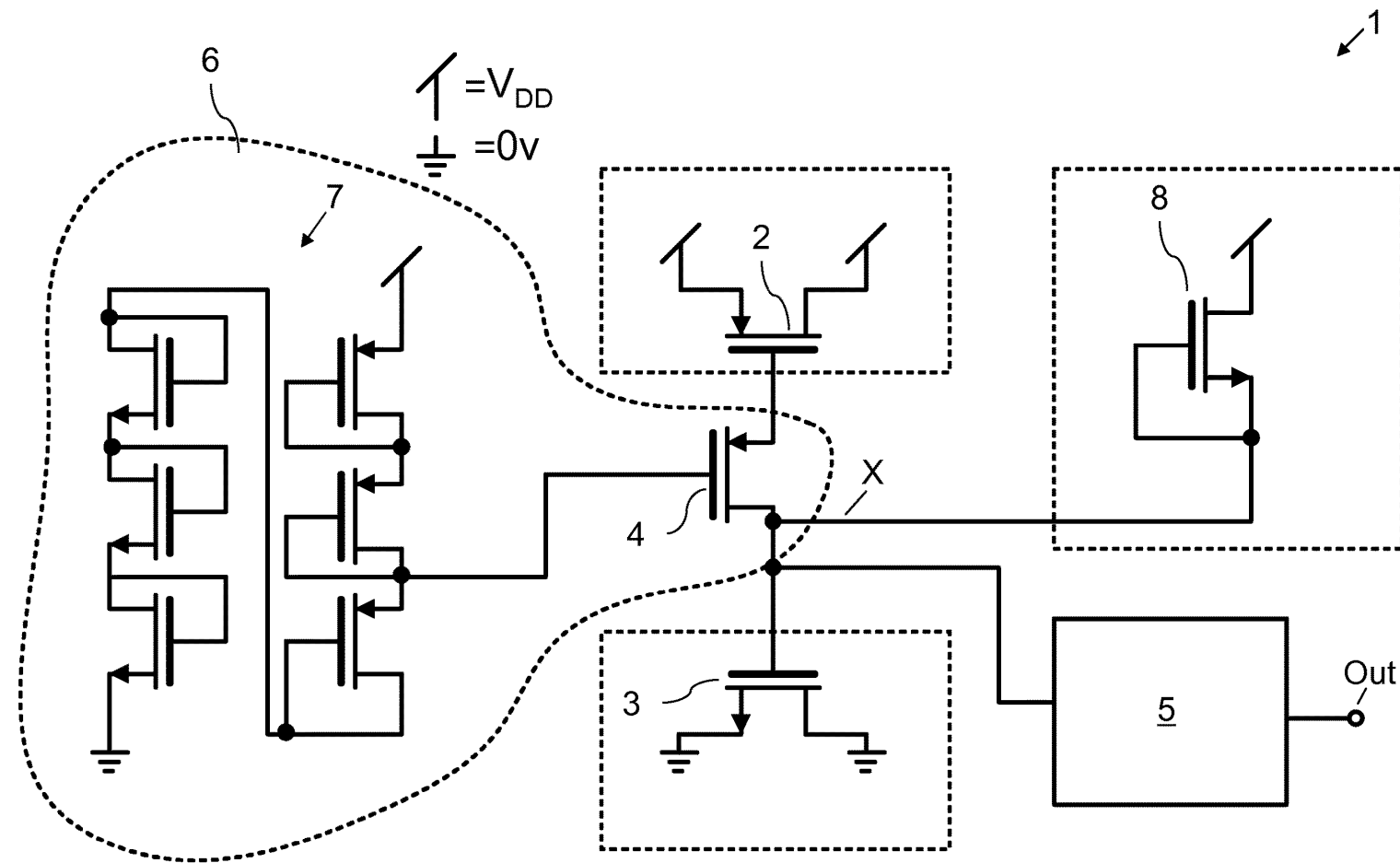



Figure 1

ESD

# Electrostatic Discharge

If you make an IC, you must consider Electrostatic Discharge (ESD) Protection circuits

Standards for testing at [JEDEC](#)

 

## ESD in Silicon Integrated Circuits

Second Edition

AJITH AMERASEKERA | CHARVAKA DUVVURY



# When do ESD events occur?

**Before/during PCB**

**Human body model (HBM)**

**Charged device model  
(CDM)**


**After PCB**

**Human body model (HBM)**

**System level ESD**
 
# Human body model (HBM)


- Models a person touching a device with a finger
- **Long** duration (around 100 ns)
- Acts like a current source into a pin
- Can usually be handled in the I/O ring
- 4 kV HBM ESD is 2.67 A peak current



 
# Charged device model (CDM)

Assume there is an equal number of electrons and protons on the IC.  
According to Gauss' law

$$\oint_{\partial\Omega} \mathbf{E} \cdot d\mathbf{S} = \frac{1}{\epsilon_0} \iiint_V \rho \cdot dV$$




$$t = 0^-$$

 


→

$$t = 0^+$$

 

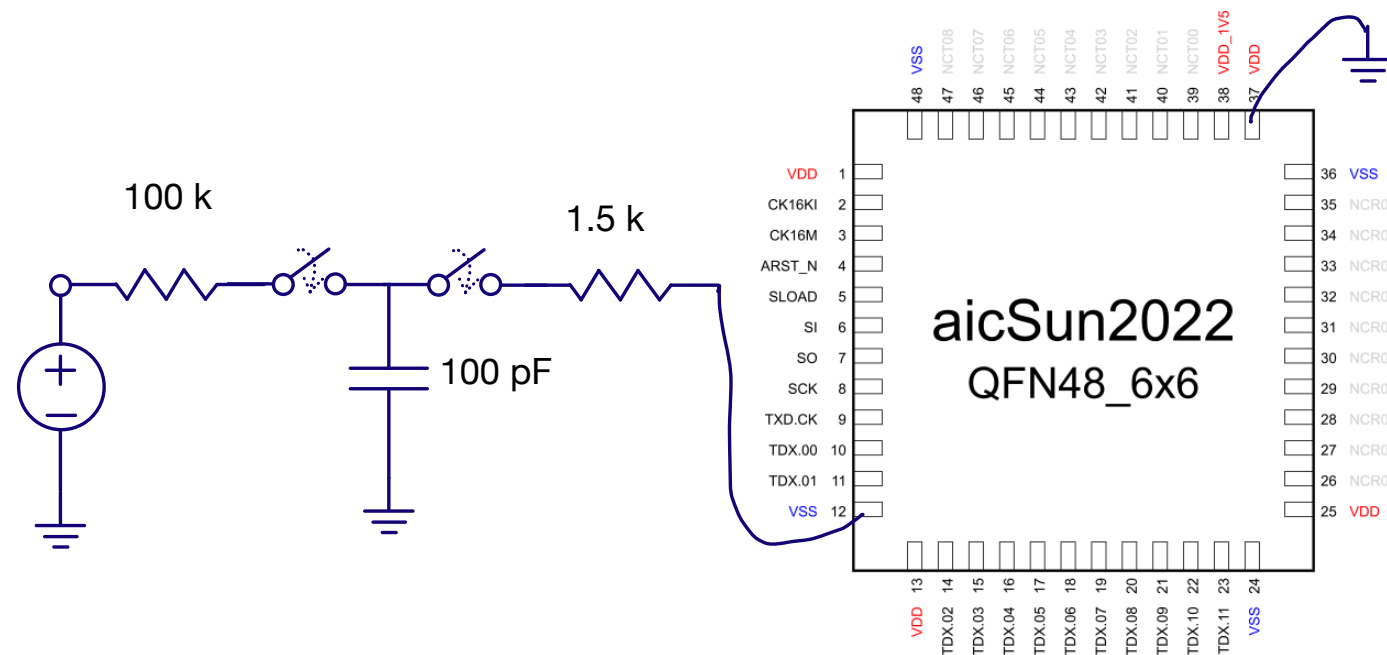
# An HBM ESD zap example


Imagine a ESD zap between VSS and VDD. How can we protect the device?




# Permutations

0 → 1	VSS → VDD
1 → 0	VDD → VSS
0 → 2	VSS → PIN
2 → 0	PIN → VSS
1 → 2	VDD → PIN
2 → 1	PIN → VDD

 


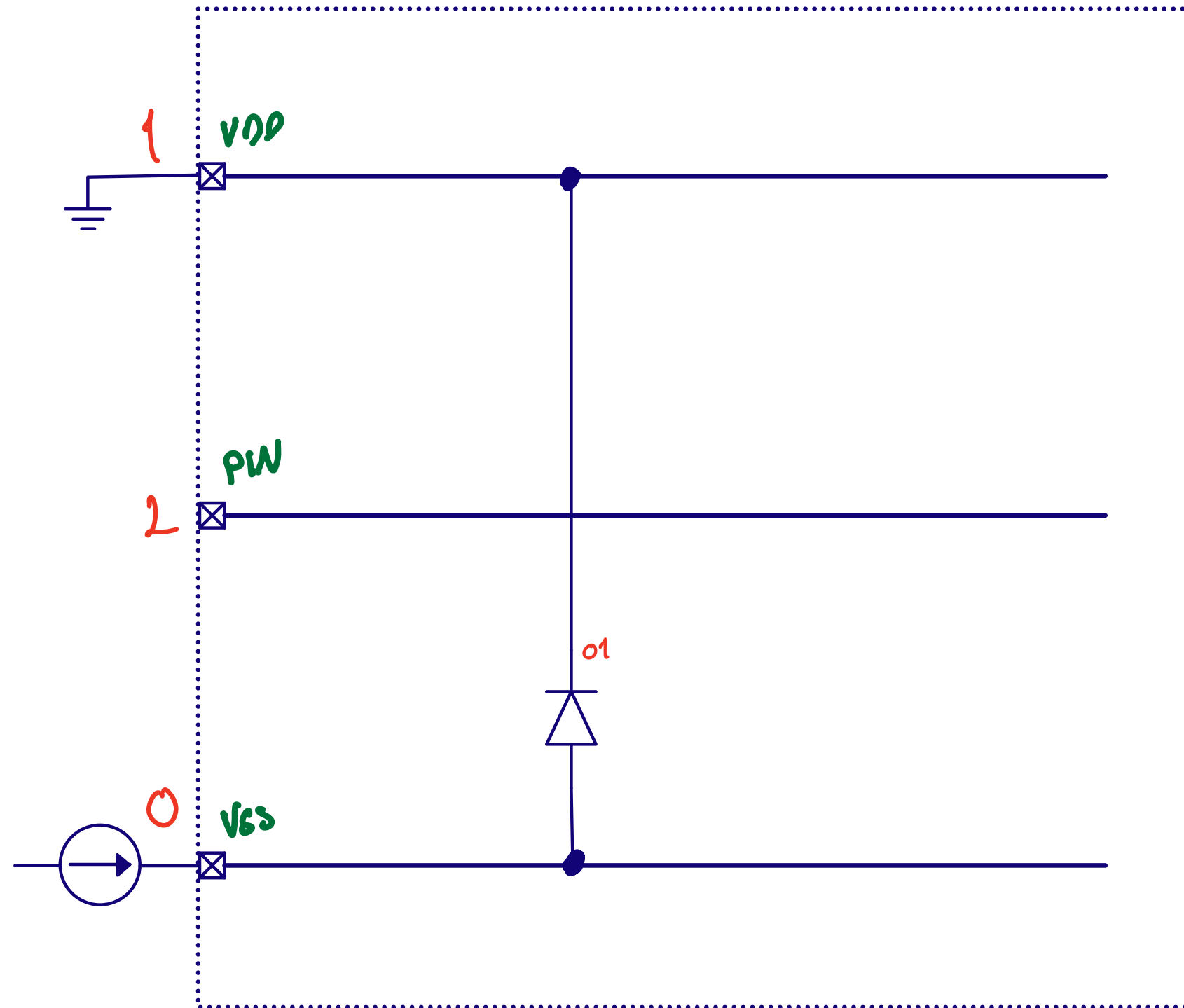


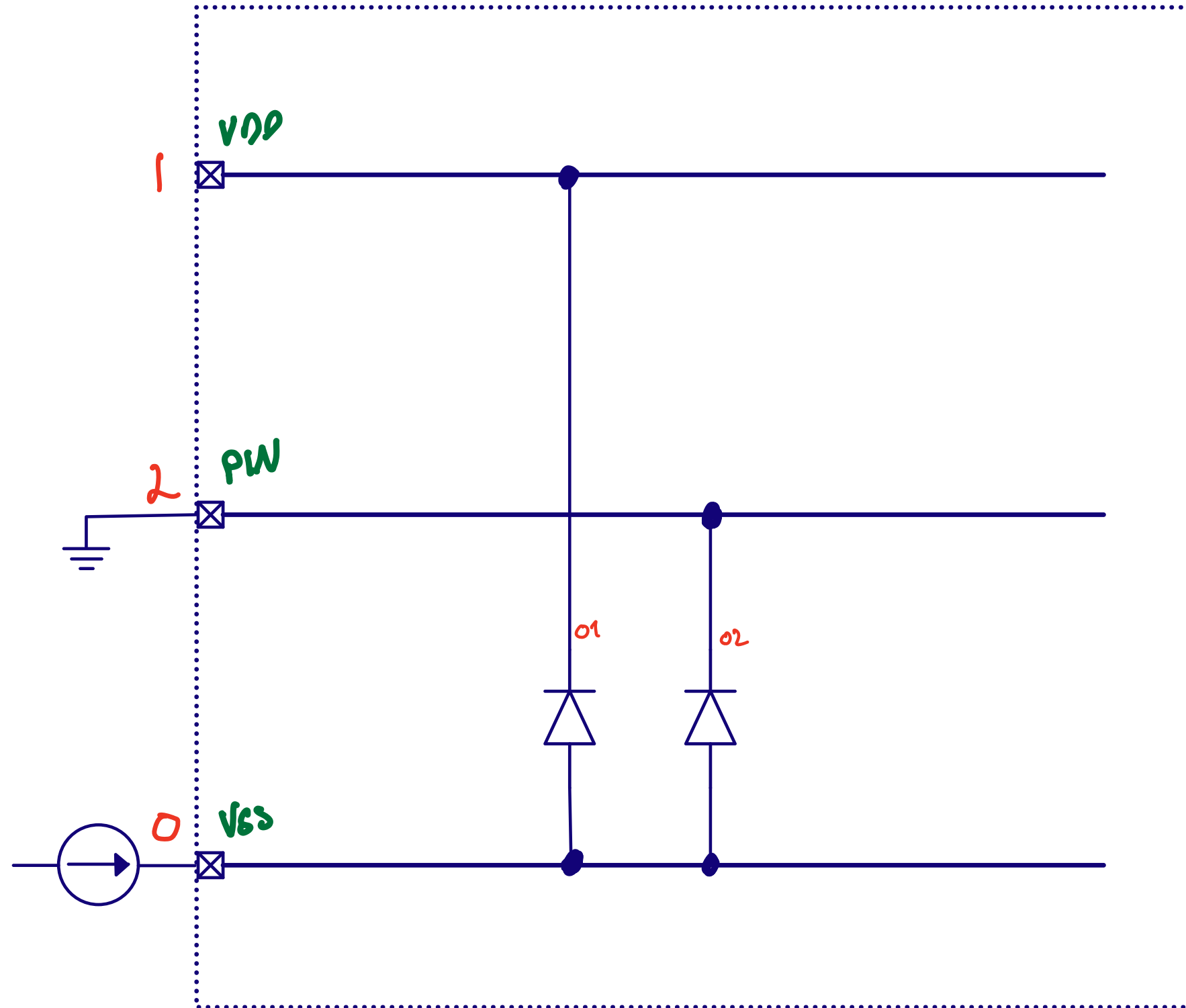



 
~~0 → 1 = 01~~  
~~1 → 0 = 10~~  
~~0 → 2 = 02~~  
~~2 → 0 = 20~~  
~~1 → 2 = 12~~  
~~2 → 1 = 21~~



 

2,6 A

Why does this work?

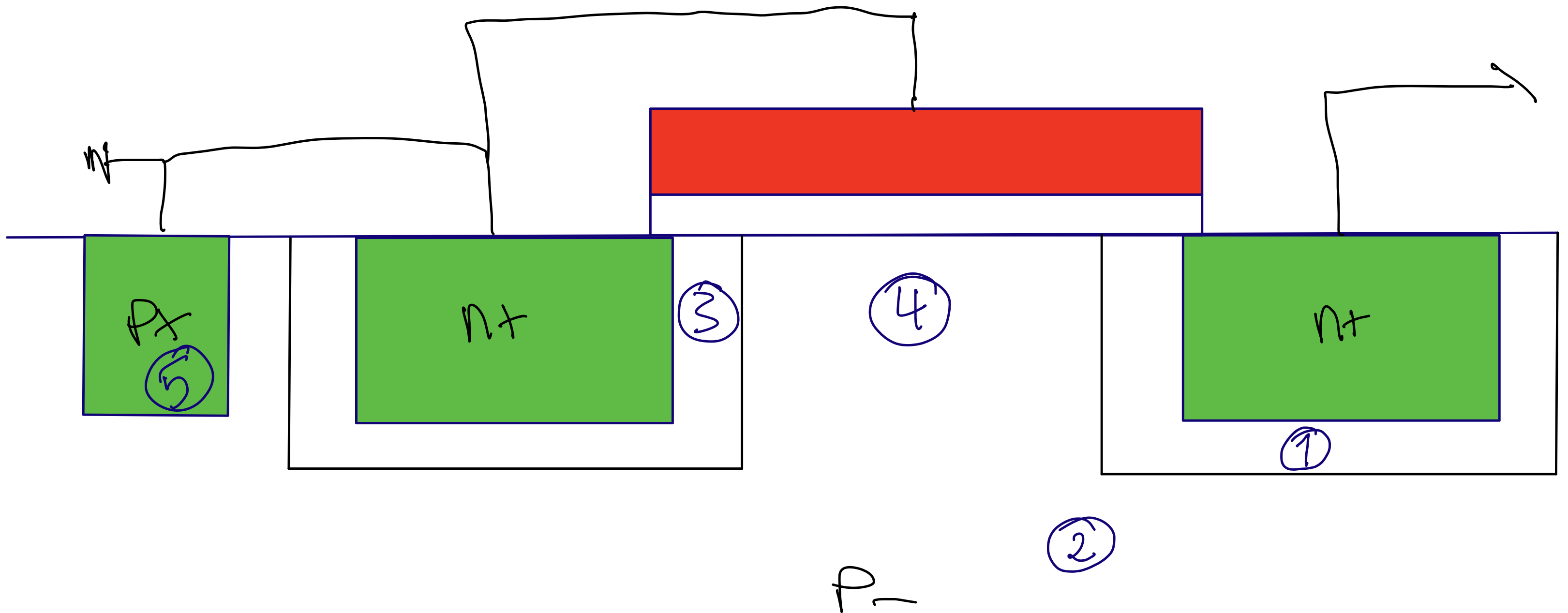


If you don't do the layout right

New Ballasting Layout Schemes to Improve ESD Robustness of I/O Buffers in Fully Silicided CMOS Process

But I just want a digital input, what  
do I need?

Bondwire

 


Pad


Primary ESD

Secondary ESD

Input Buffer

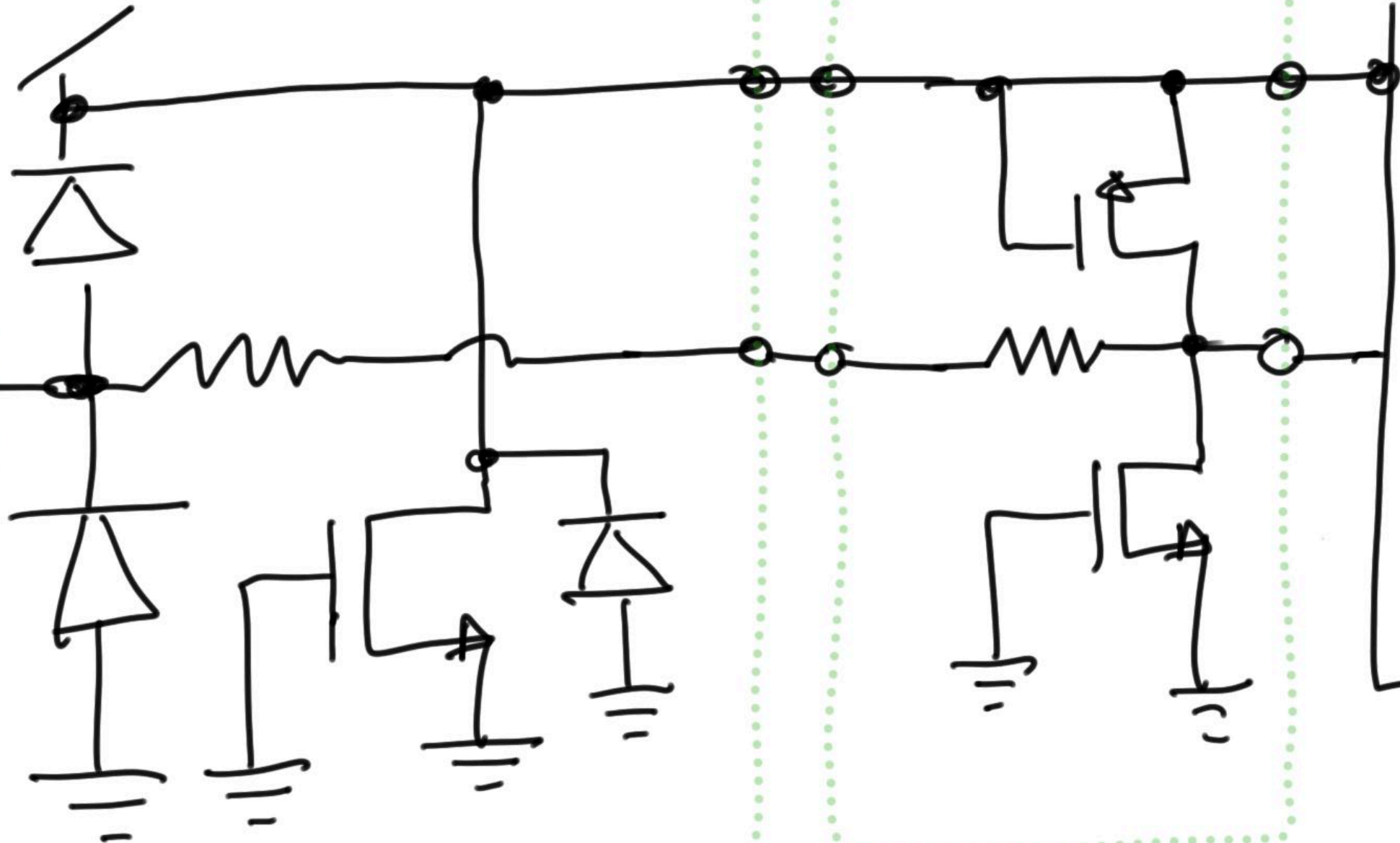

# Input buffer

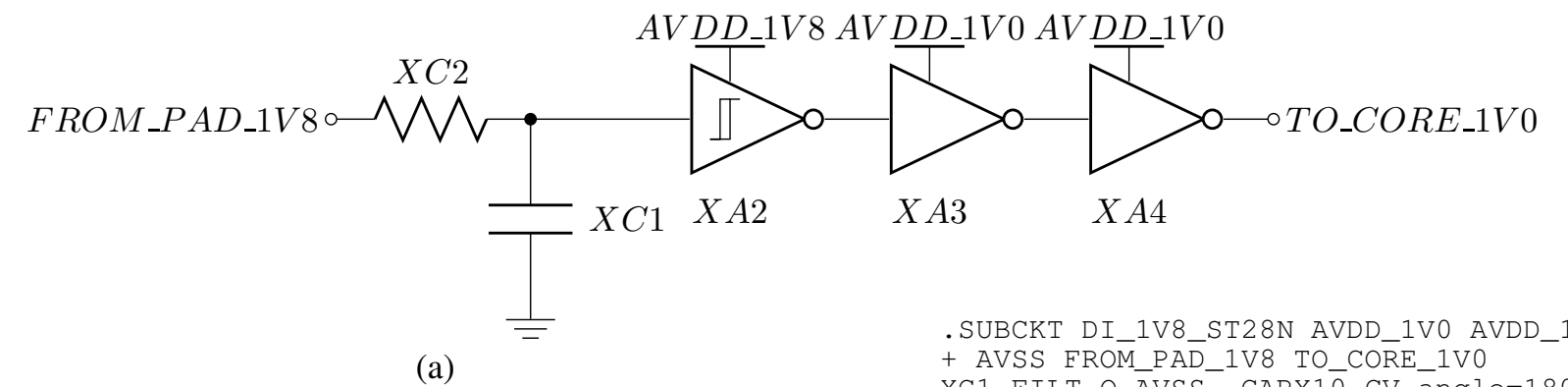

```
.SUBCKT DI_1V8_ST28N AVDD_1V0 AVDD_1V8
+ AVSS FROM_PAD_1V8 TO_CORE_1V0
XC1 FILT_O AVSS CAPX10_CV angle=180
XC2 FROM_PAD_1V8 FILT_O AVSS RPPO_S0
+ xoffset=25 yoffset=15
```


```
XA5 AVSS TAPCELL_EV xoffset=20
XA2 FILT_O SCHMITT_O AVDD_1V8 AVSS SCX1_EV
```

```
XA5a AVSS TAPCELL_EV yoffset=20
XA3 SCHMITT_O INV_O AVDD_1V0 AVSS IVX1_EV
```

```
XA4 INV_O TO_CORE_1V0 AVDD_1V0 AVSS IVX8_CV
+ yoffset=15
XA6 AVSS TAPCELL_CV
```

```
.ENDS
```

(b)

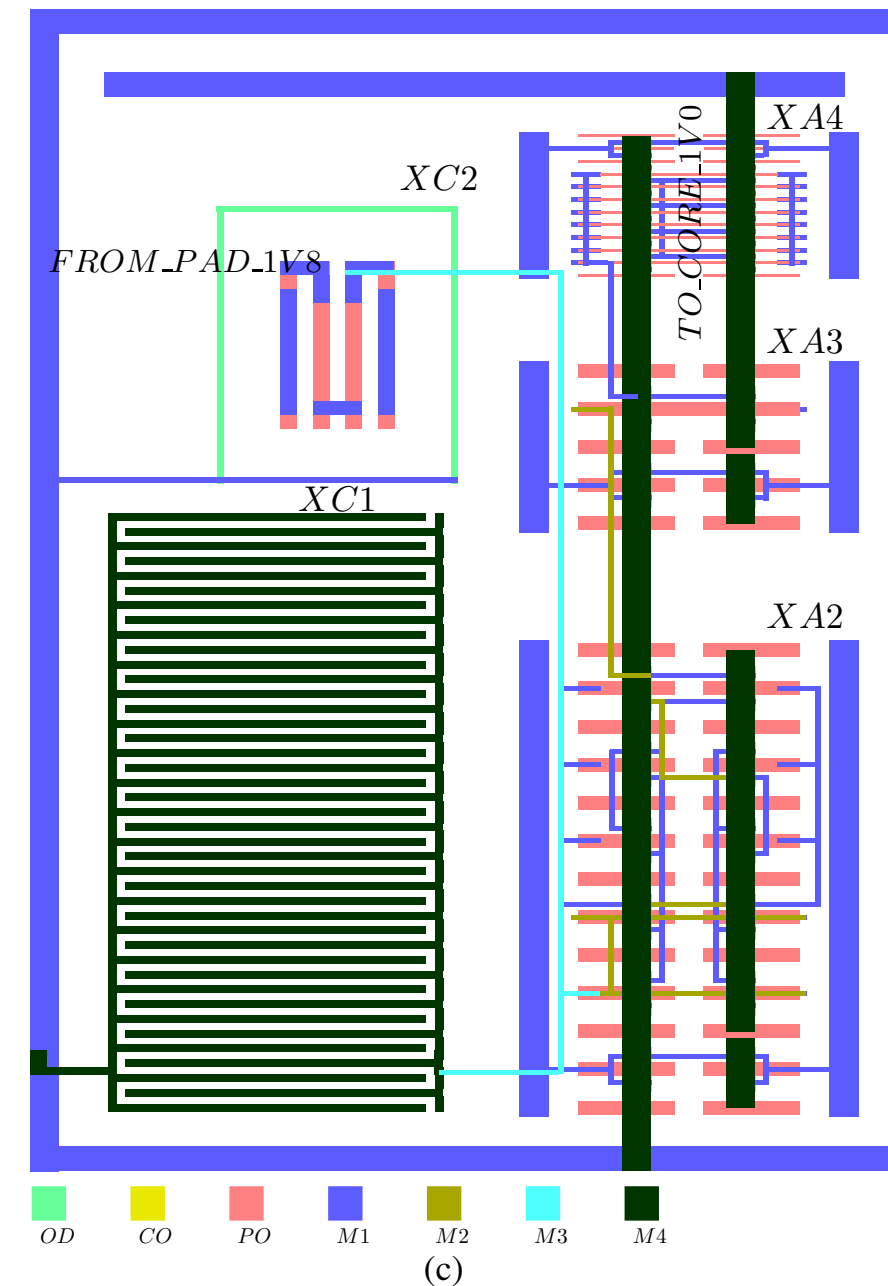


```
{ "name" : "DI_1V8_ST28N",
  "boundaryIgnoreRouting" : 0,
  "composite" : 1, "noPowerRoute" : 1,
  "schematic" : 0,
  "class" : "Layout::LayoutDigitalCell",
  "afterPlace" : {
    "addPowerRings" : [
      ["M1", "AVDD_1V0", "t"],
      ["M1", "AVSS", "btrl"]
    ]
  },
  "beforeRoute" : {
    "addPowerConnections" : [
      ["AVDD_1V0", "XA", "top"],
      ["AVSS", "XC", "left"],
      ["AVSS", "XA4|XA2", "bottom"]
    ],
    "addConnectivityRoutes" : [
      ["M3", "FILT_O", "--|-", "onTopR"],
      ["M2", "SCHMITT_O", "-|---"],
      ["M1", "INV_O", "-|---"]
    ]
  }
}
```

(d)

# Latch-up




 


How can current in one place lead to a current somewhere else?

Logic cells close to large NMOS pad drivers are prone to latch-up.

 
The latch-up process can start with electrons injected into the p-type substrate.



 1. Electrons injected into substrate, diffuse around, but will be accelerated by n-well to p-substrate built in voltage. Can end up in n-well
2. PMOS drain can be forward biased by reduced n-well potential. Hole injection into n-well. Holes diffuse around, but will be accelerated by n-well to p-substrate built in voltage. Can end up in p-substrate under NMOS
3. NMOS source pn-junction can be forward biased. Electrons injected into p-substrate. Diffuse around, but will be accelerated by n-well to p-substrate built in voltage.
4. Go to 2 (latch-up)





 





You must **always handle ESD** on an IC

- Do everything yourself
- Use libraries from foundry
- Get help [www.sofics.com](http://www.sofics.com)

# Thanks!